

MultiCycle CPU




中国科学院
INSTITUTE OF COMPUTING TECHNOLOGY


University of Chinese Academy of Sciences (UCAS)

Why a Multiple Cycle CPU?

 - The problem => single-cycle cpu has a cycle time long enough to complete the **longest** instruction in the machine
- The solution => break up execution into smaller tasks, each task taking a cycle, different instructions requiring different numbers of cycles or tasks
- Other advantages => reuse of functional units (e.g., alu, memory)
- $ET = IC * CPI * CT$



High Level View

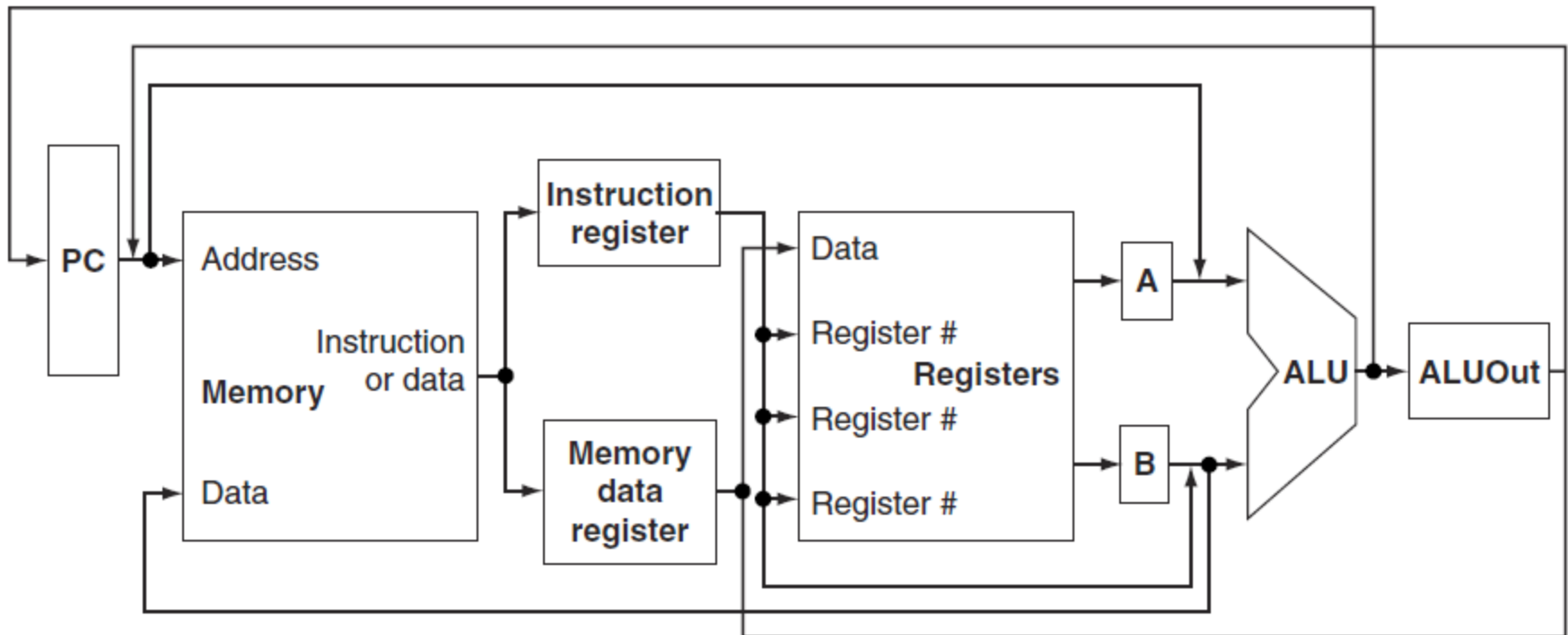

- A **single memory unit** is used for both instructions and data.
- There is **a single ALU**, rather than an ALU and two adders.
- **One or more registers** are added after every major functional unit to hold the output of that unit until the value is used in a subsequent clock cycle

Breaking Execution into Clock Cycles


- We will have five execution steps (not all instructions use all five)
 - Fetch
 - Decode & register fetch
 - Execute
 - Memory access
 - Write-back
- We will use Register-Transfer-Language (RTL) to describe these steps

Breaking Execution into Clock Cycles




- Introduces extra registers when:
 - Signal is **computed** in one clock cycle and **used** in another, AND
 - The inputs to the functional block that outputs this signal can **change** before the signal is written into a state element.
- Significantly complicates control. **Why?**
- The goal is to **balance** the amount of work done each cycle.

Multi-Cycle Datapath

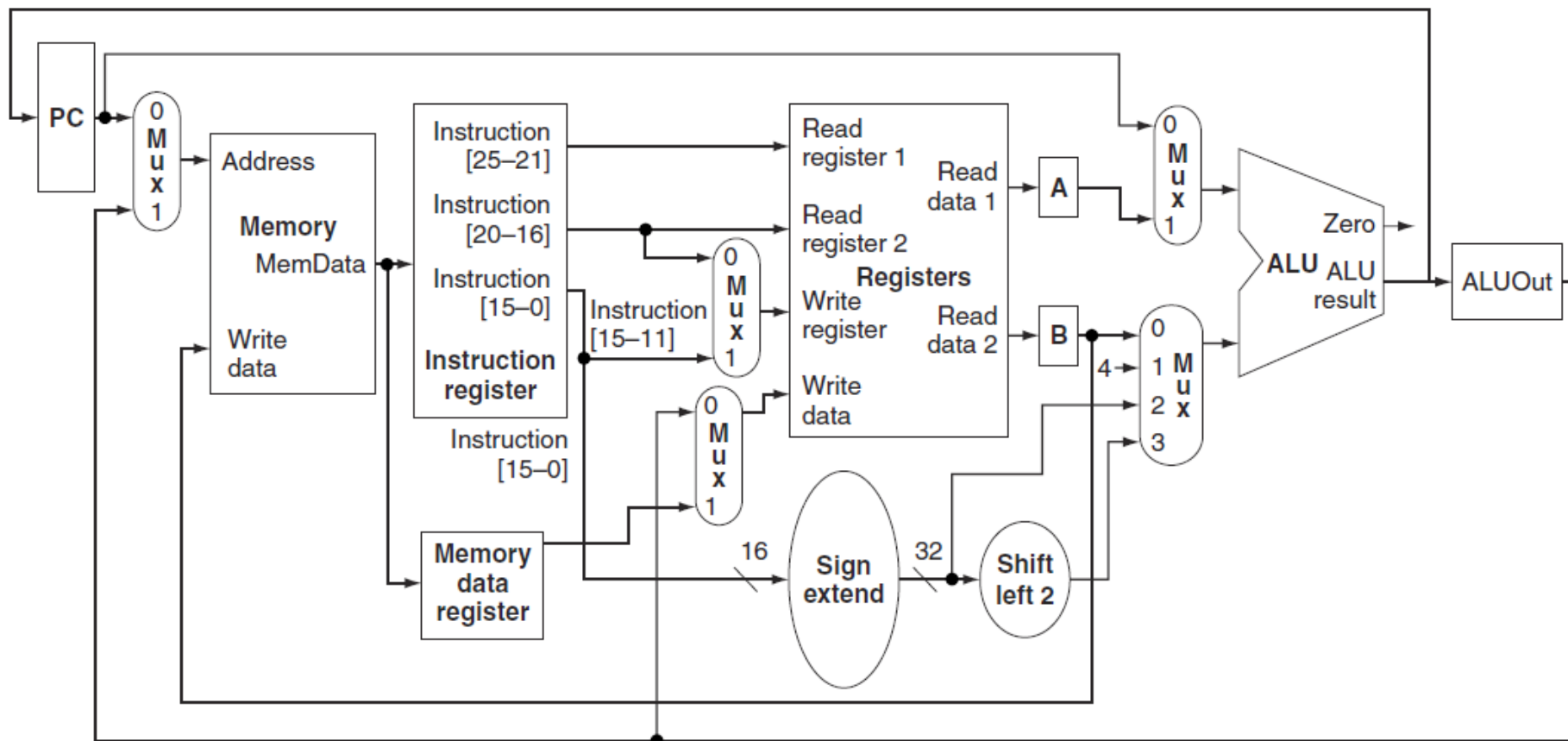


- Intermediate latches
- One ALU
- One memory

Multicycle Datapath with Control Signals

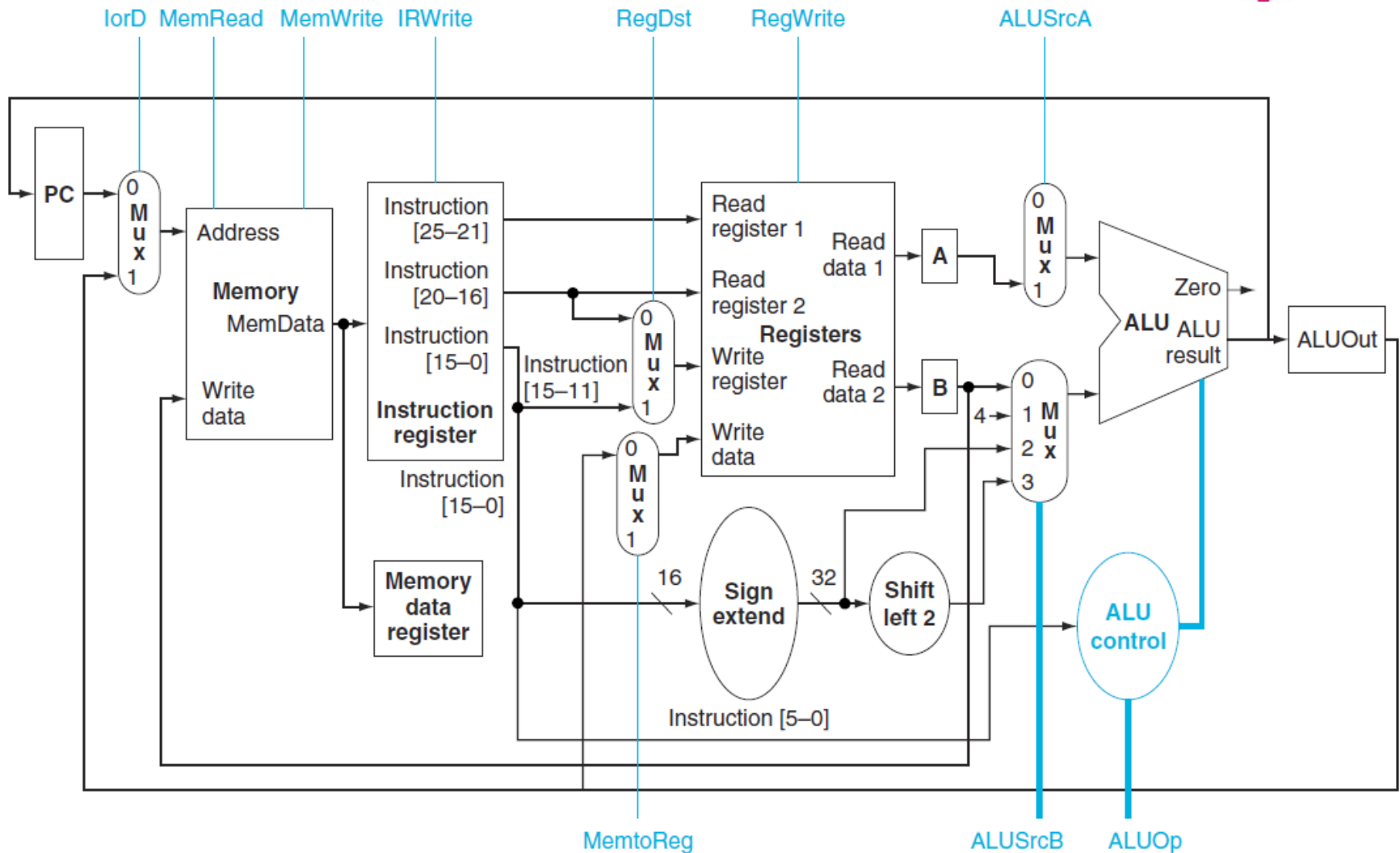

Control Unit

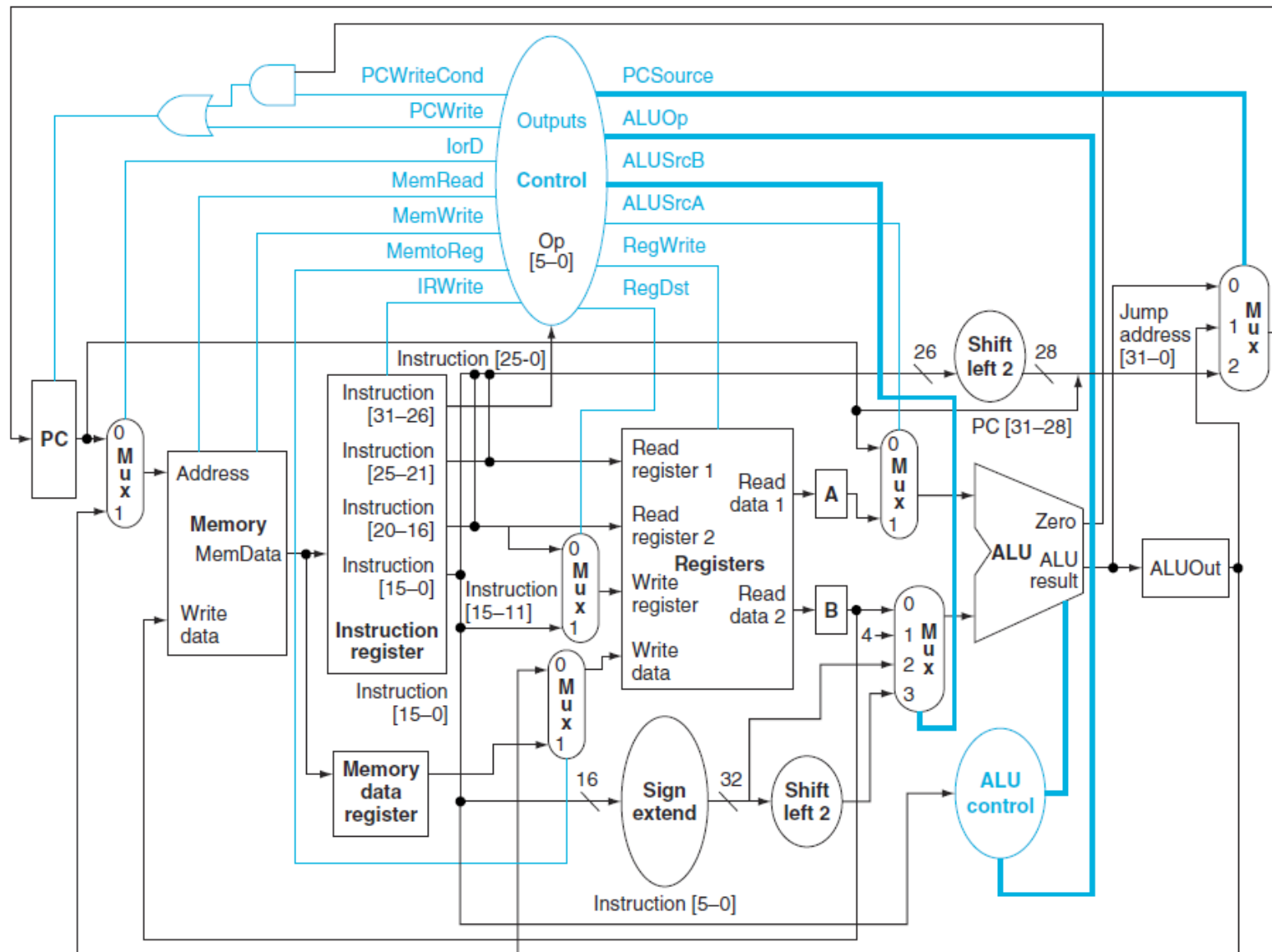

Actions of Control Signals



| Signal name | Effect when deasserted | Effect when asserted |
|-------------|--|---|
| RegDst | The register file destination number for the Write register comes from the rt field. | The register file destination number for the Write register comes from the rd field. |
| RegWrite | None. | The general-purpose register selected by the Write register number is written with the value of the Write data input. |
| ALUSrcA | The first ALU operand is the PC. | The first ALU operand comes from the A register. |
| MemRead | None. | Content of memory at the location specified by the Address input is put on Memory data output. |
| MemWrite | None. | Memory contents at the location specified by the Address input is replaced by value on Write data input. |
| MemtoReg | The value fed to the register file Write data input comes from ALUOut. | The value fed to the register file Write data input comes from the MDR. |
| lorD | The PC is used to supply the address to the memory unit. | ALUOut is used to supply the address to the memory unit. |
| IRWrite | None. | The output of the memory is written into the IR. |
| PCWrite | None. | The PC is written; the source is controlled by PCSource. |
| PCWriteCond | None. | The PC is written if the Zero output from the ALU is also active. |

| Signal name | Value (binary) | Effect |
|-------------|----------------|---|
| ALUOp | 00 | The ALU performs an add operation. |
| | 01 | The ALU performs a subtract operation. |
| | 10 | The funct field of the instruction determines the ALU operation. |
| ALUSrcB | 00 | The second input to the ALU comes from the B register. |
| | 01 | The second input to the ALU is the constant 4. |
| | 10 | The second input to the ALU is the sign-extended, lower 16 bits of the IR. |
| | 11 | The second input to the ALU is the sign-extended, lower 16 bits of the IR shifted left 2 bits. |
| PCSource | 00 | Output of the ALU ($PC + 4$) is sent to the PC for writing. |
| | 01 | The contents of ALUOut (the branch target address) are sent to the PC for writing. |
| | 10 | The jump target address ($IR[25:0]$ shifted left 2 bits and concatenated with $PC + 4[31:28]$) is sent to the PC for writing. |

Breaking the Instruction Execution into Clock Cycles

1. Fetch

- $IR = Mem[PC]$
- $PC = PC + 4$
- *May not be final value of PC*

2. Instruction Decode and Register Fetch

- $A = \text{Reg}[\text{IR}[25-21]]$
- $B = \text{Reg}[\text{IR}[20-16]]$
- $\text{ALUOut} = \text{PC} + (\text{sign-extend}(\text{IR}[15-0]) \ll 2)$
- Compute target before we know if it will be used (may not be branch, branch may not be taken)
- **ALUOut** is a new state element (temp register)
- Everything up to this point must be **Instruction-independent**, because we still haven't decoded the instruction.
- Everything instruction (opcode)-dependent from here on.

3. Execution, Memory Address Computation, or Branch Completion

- Memory reference (load or store)
 - $ALUOut = A + \text{sign-extend}(IR[15-0])$
- R-type
 - $ALUOut = A \text{ op } B$
- Branch
 - if $(A == B)$ $PC = ALUOut$
- *At this point, Branch is complete, and we start over; others require more cycles.*

4. Memory access or R-type completion

- Memory reference (load or store)
 - Load
 - $MDR = Mem[ALUout]$
 - Store
 - $Mem[ALUout] = B$
- R-type
 - $Reg[IR[15-11]] = ALUout$
- *R-type is complete, store is complete.*


5. Memory Write-Back (Memory Read Completion)

- $\text{Reg}[\text{IR}[20-16]] = \text{MDR}$
- *Load is complete*

Summary of Execution Steps

| Step | R-type | Memory | Branch |
|---|---|---|---------------------------------------|
| Instruction Fetch | $IR = Mem[PC]$ $PC = PC + 4$ | | |
| Instruction Decode/ register fetch | $A = Reg[IR[25-21]]$ $B = Reg[IR[20-16]]$ $ALUout = PC + (sign-extend(IR[15-0]) \ll 2)$ | | |
| Execution, address computation, branch completion | $ALUout = A \text{ op } B$ | $ALUout = A +$ sign- extend($IR[15-0]$) | if ($A == B$) then $PC = ALUout$ |
| Memory access or R- type completion | $Reg[IR[15-11]] =$ $ALUout$ | memory-data = $Mem[ALUout]$ <i>or</i> $Mem[ALUout] =$ B | |
| Write-back | | $Reg[IR[20-16]] =$ memory-data | |


Complete Multi-Cycle Datapath

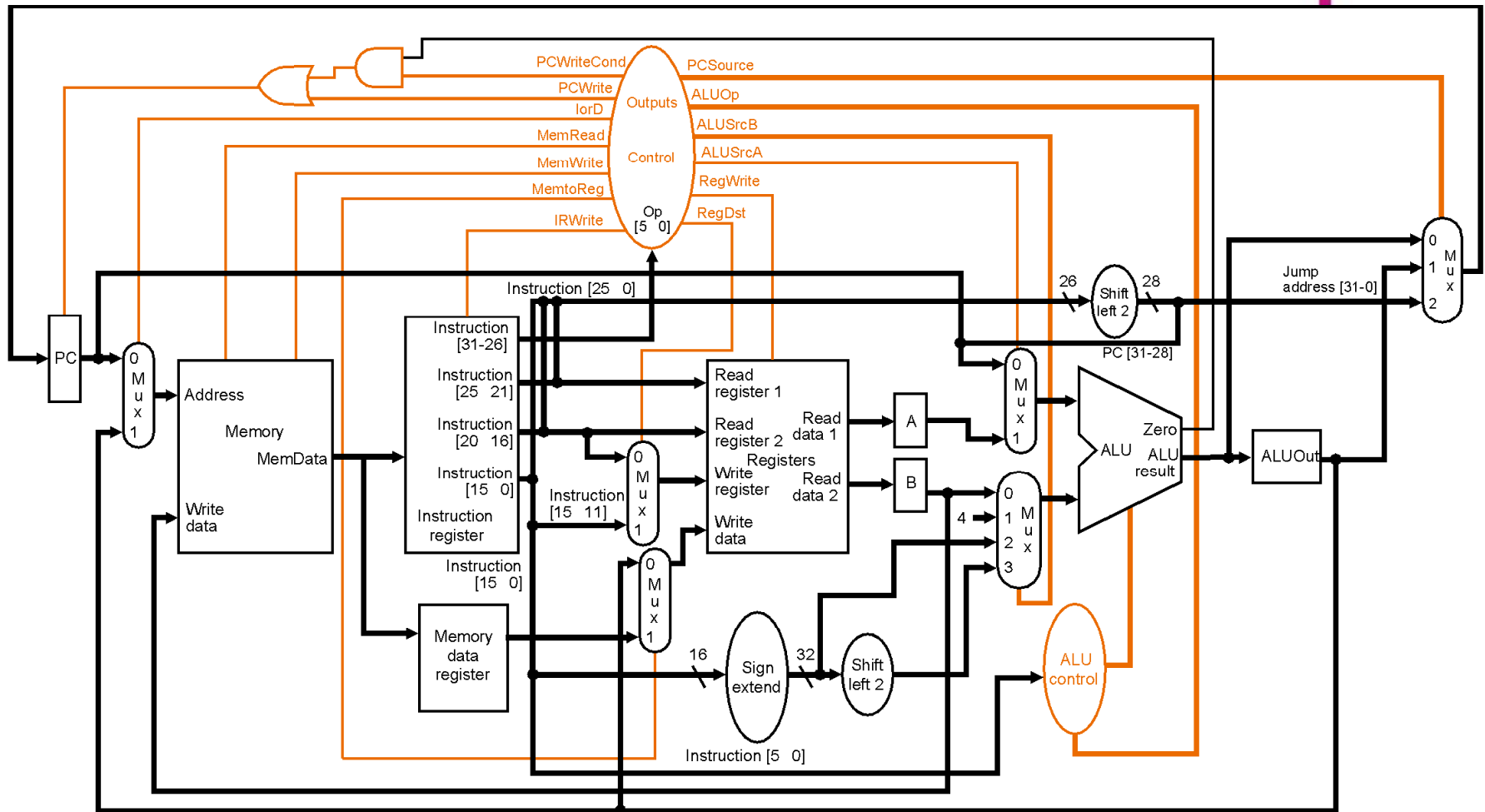

New Instruction Appears Out of Nowhere? Which One?



2. Instruction Decode and Register Fetch

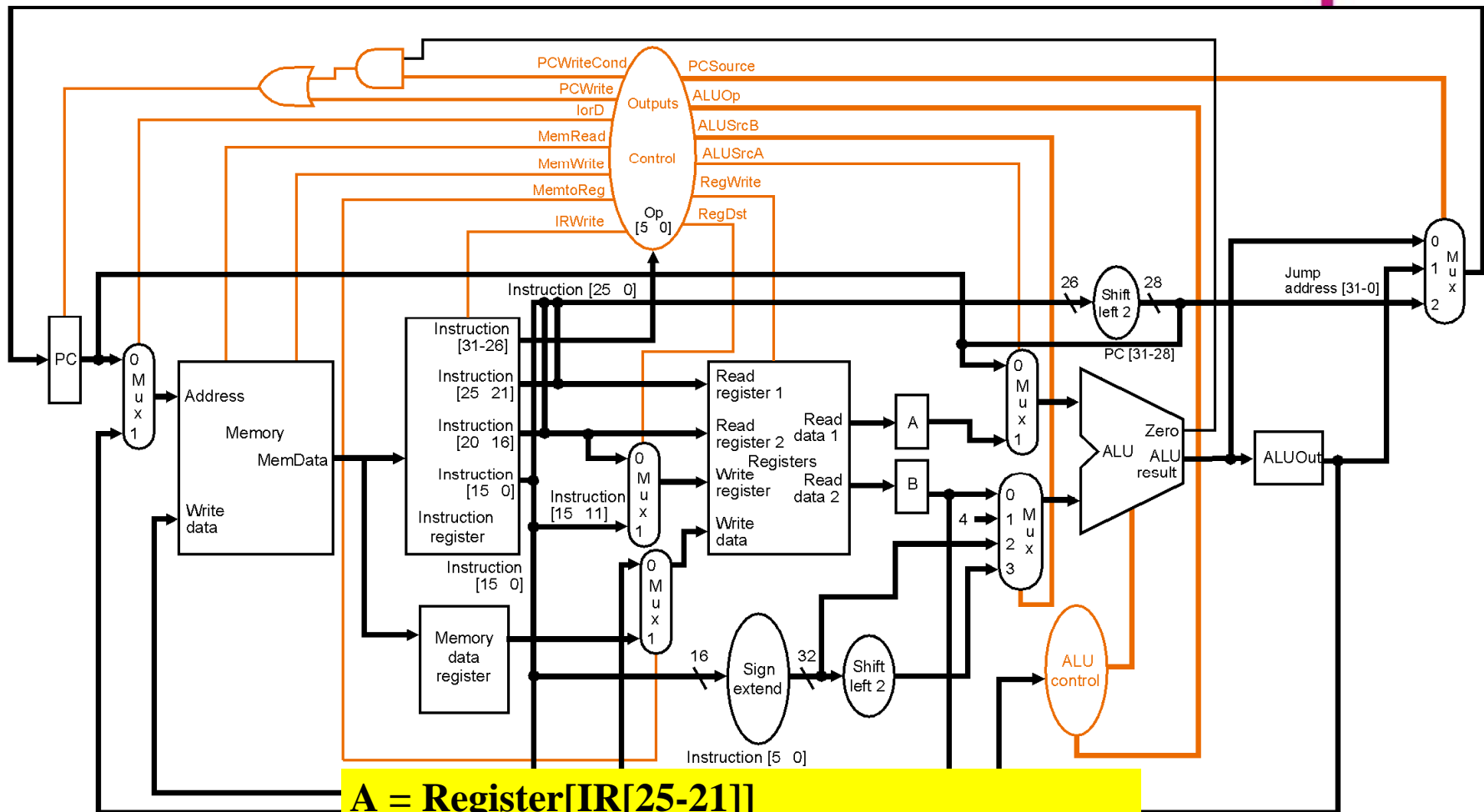


A = Register[IR[25-21]]

B = Register[IR[20-16]]


ALUOut = PC + (sign-extend (IR[15-0]) << 2)

3. Branch Completion

 


if (A == B) PC = ALUOut

3. Execution (R-Type)

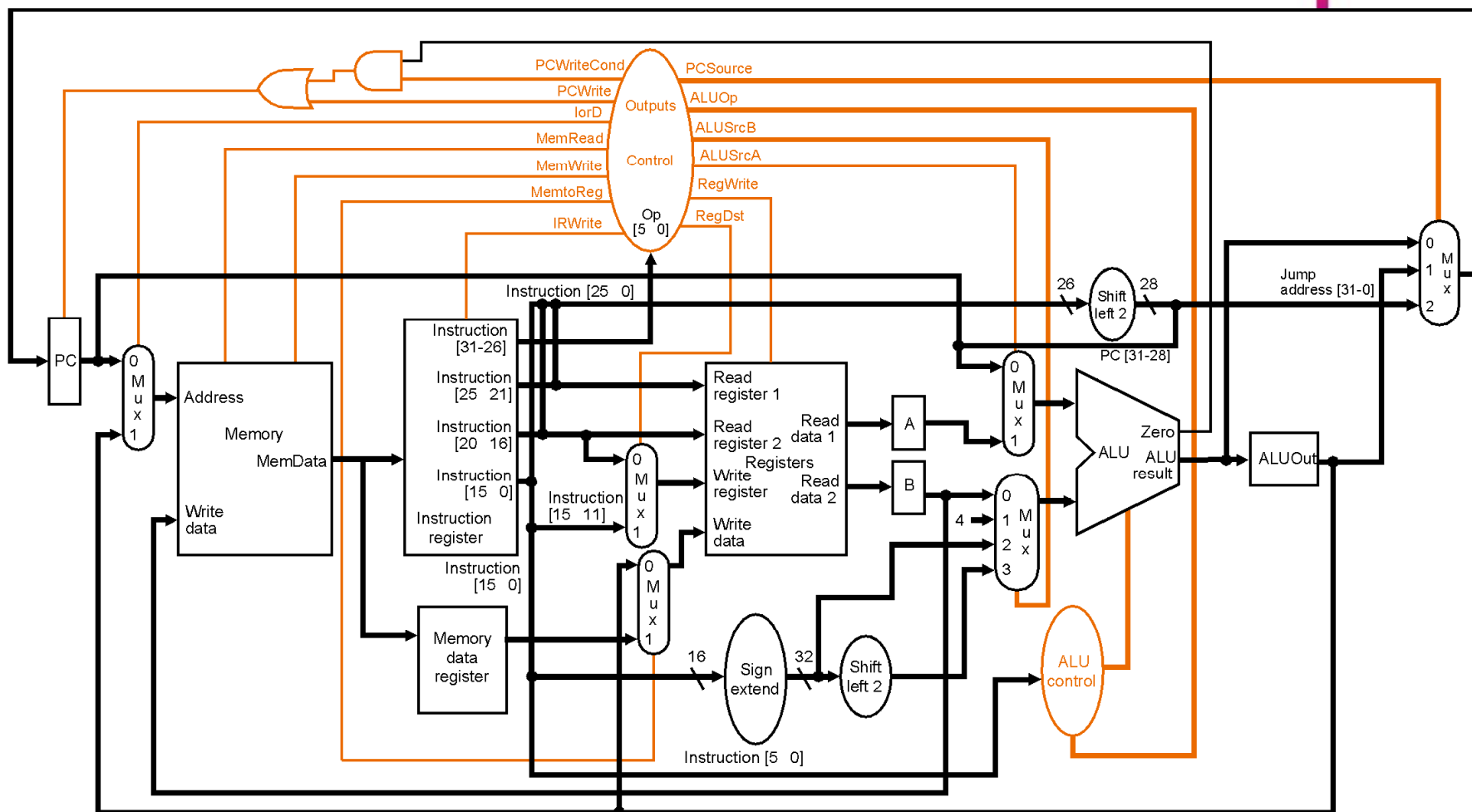


$$ALUout = A \text{ op } B$$

4. R-Type Completion

 


Reg[IR[15-11]] = ALUout

3. Memory Address Computation

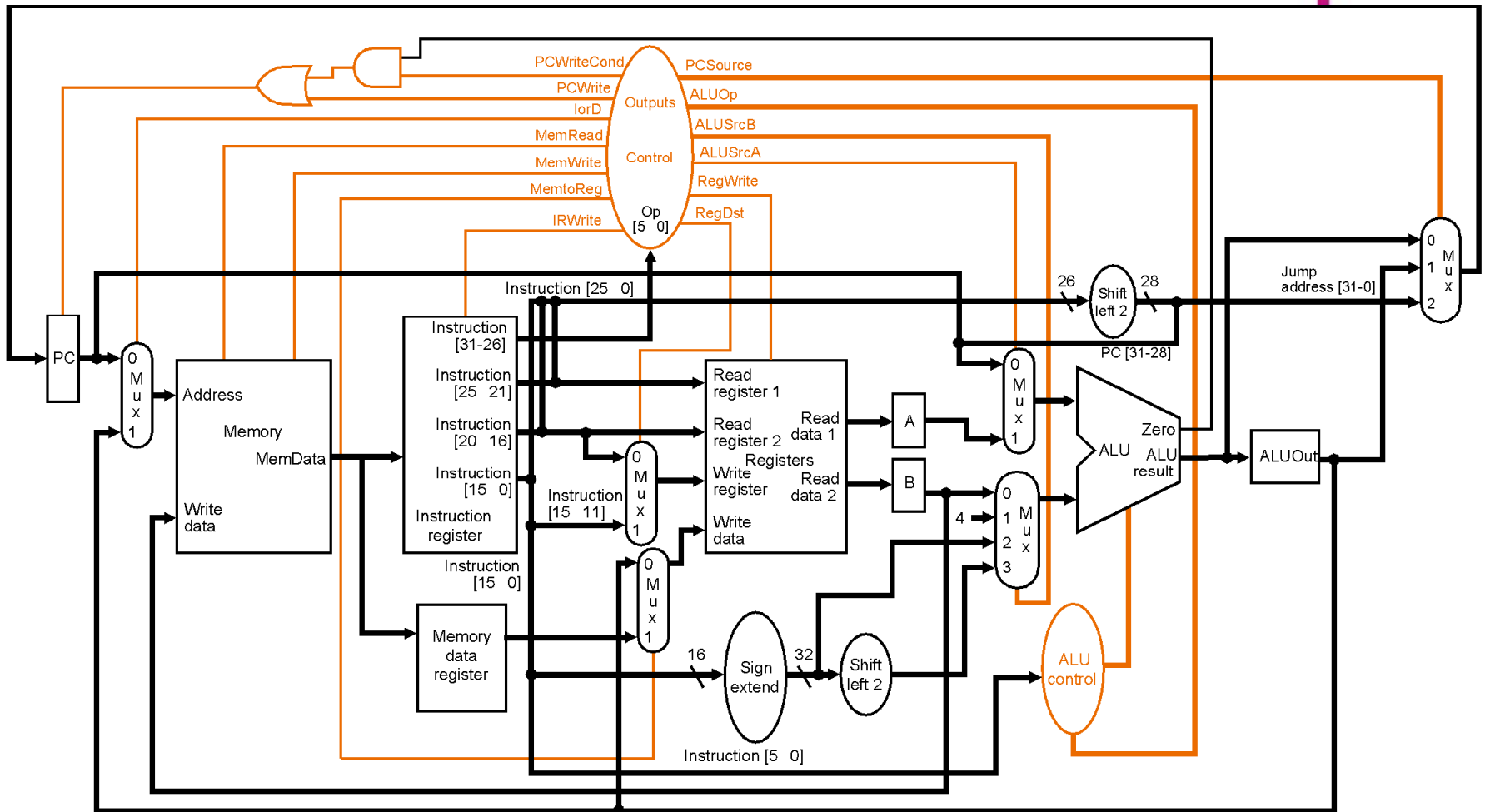


$$\text{ALUout} = A + \text{sign-extend}(\text{IR}[15-0])$$

4. Memory Access Load

 


memory-data = Memory[ALUout]

4. Memory Access Store

 


Memory[ALUout] = B

 


What About the Control?

- Single-cycle control used **combinational logic**
- What does Multi-cycle control use?
 - **FSM** defines a succession of states, **transitions** between states (based on inputs), and outputs (based on state)
 - First two states **same** for every instruction, **next state depends on opcode**


Multi-Cycle Control FSM

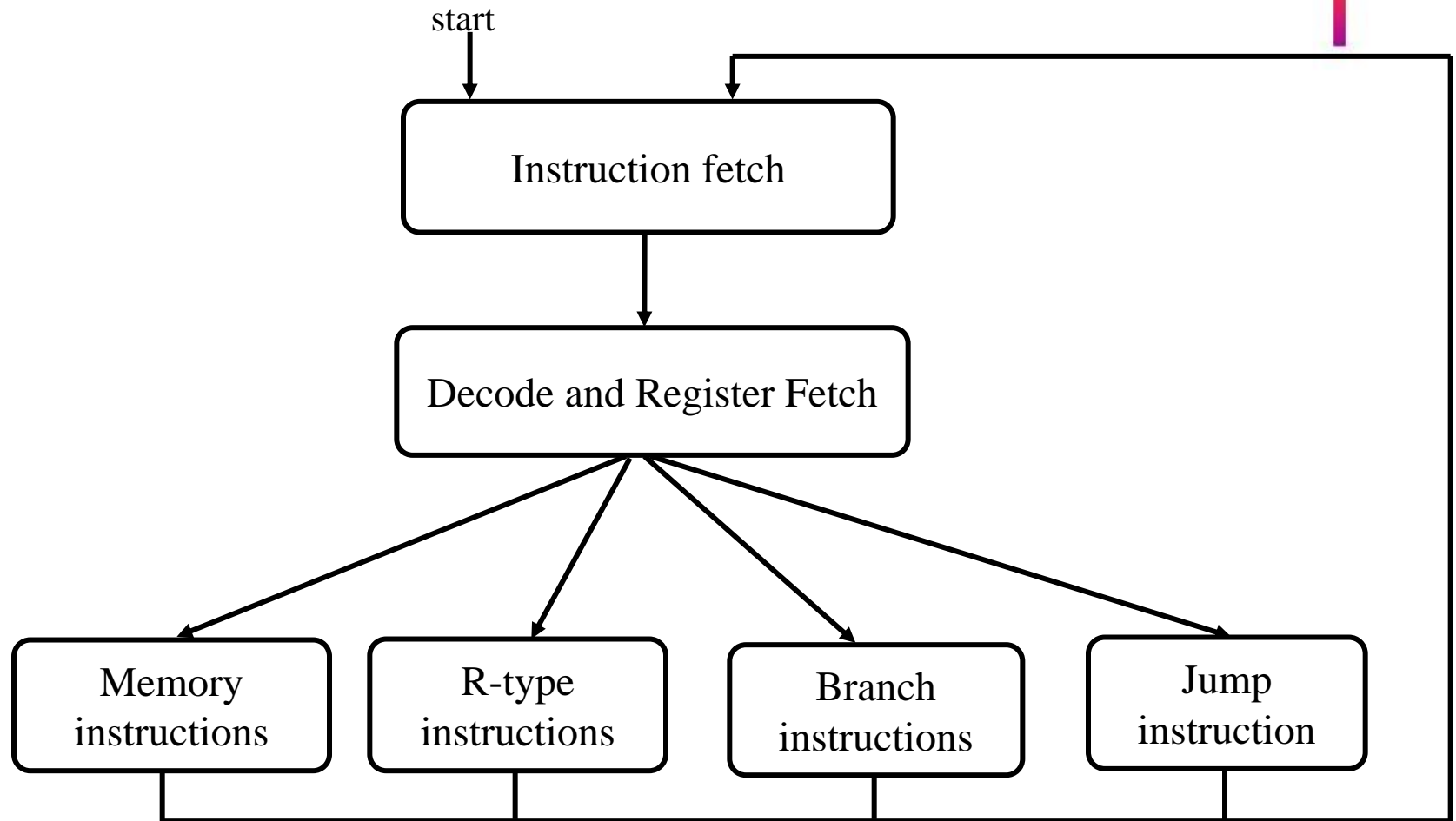


First two states of the FSM

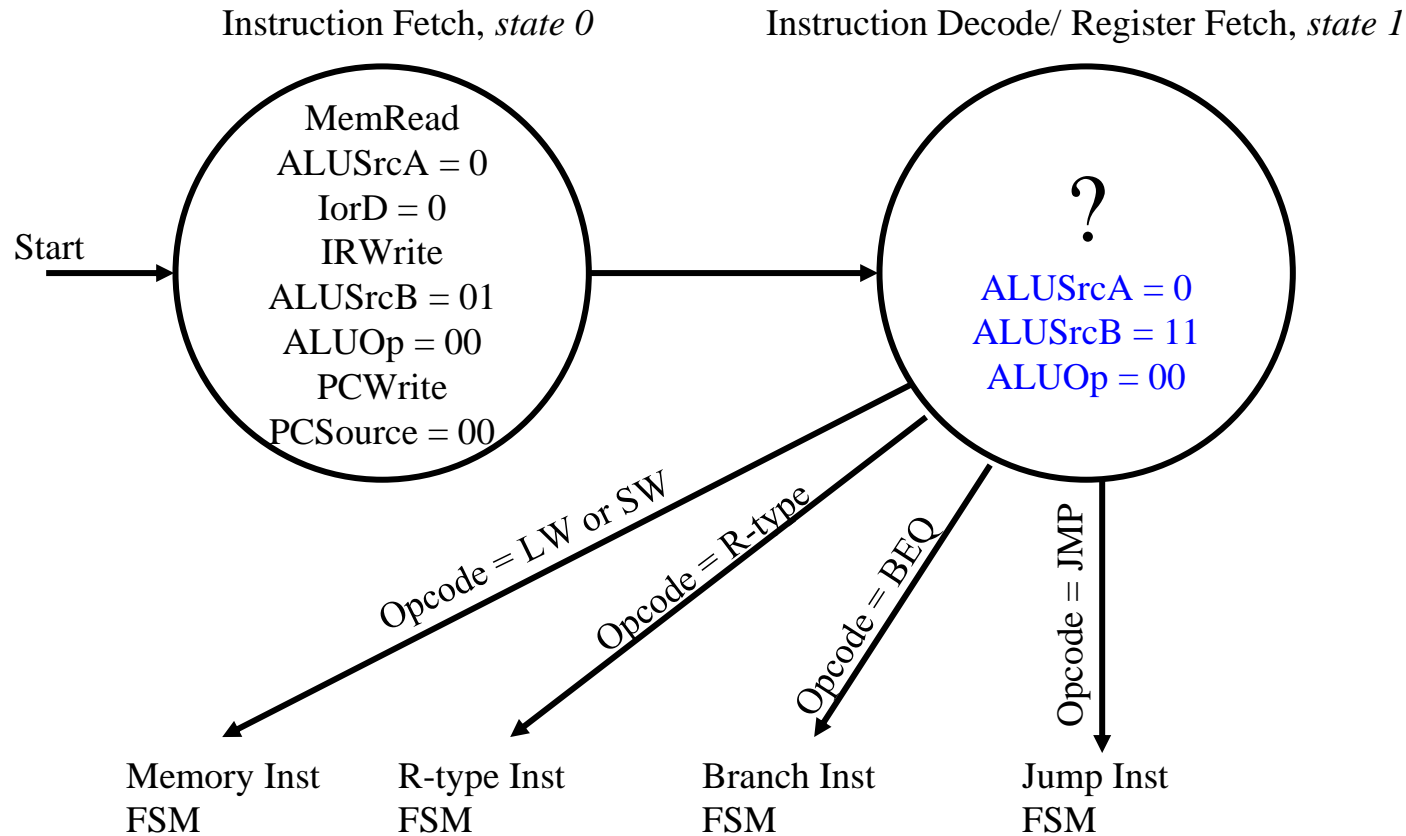


R-type Instructions

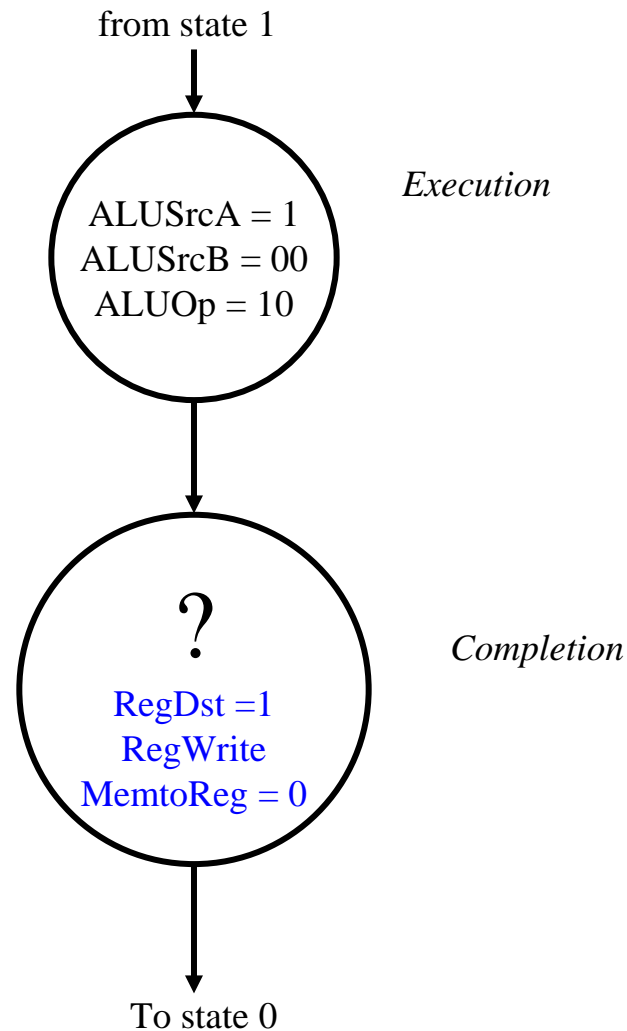


BEQ Instruction

 


Memory Instructions

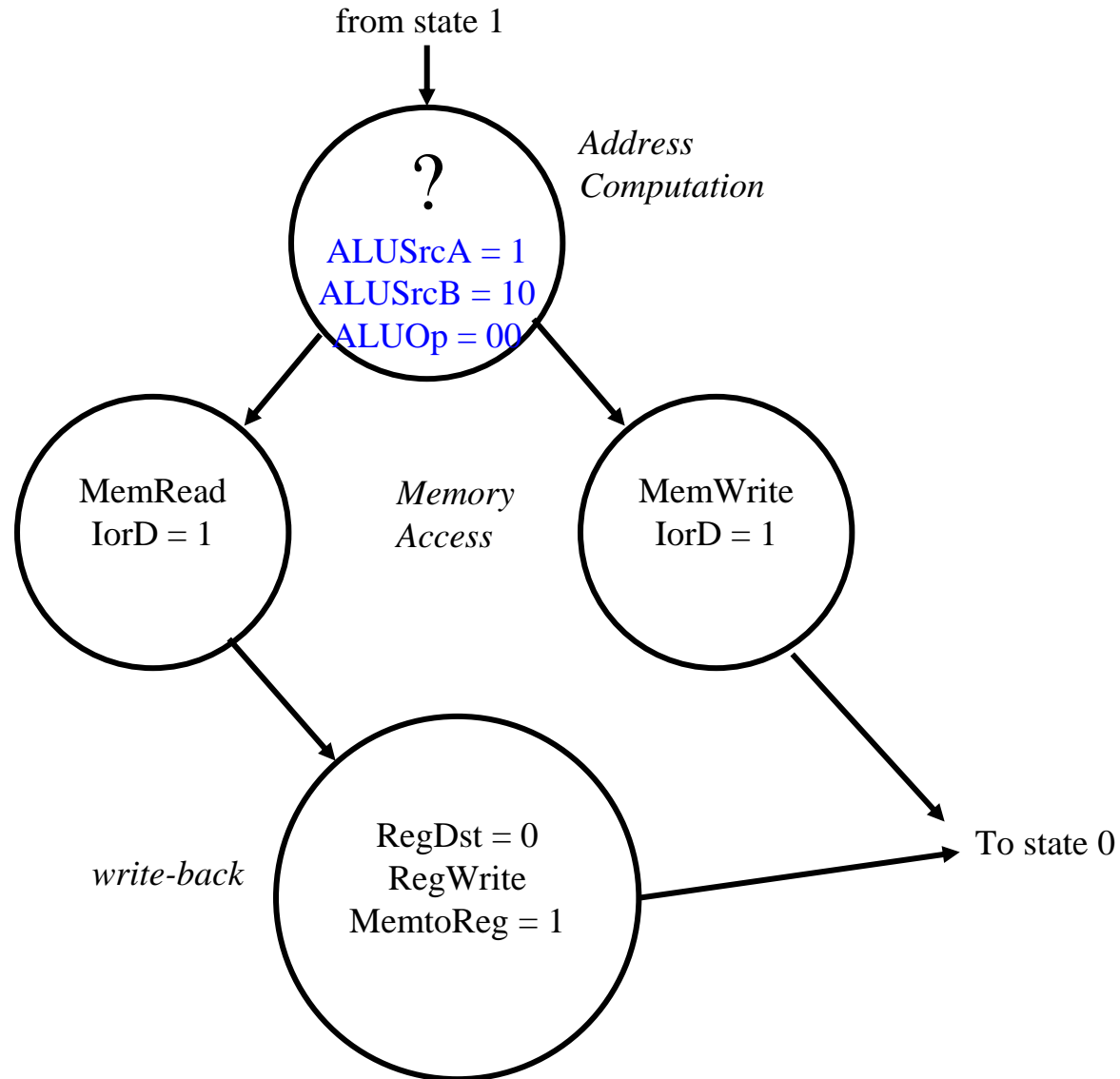

JMP Instruction

 


The Whole FSM

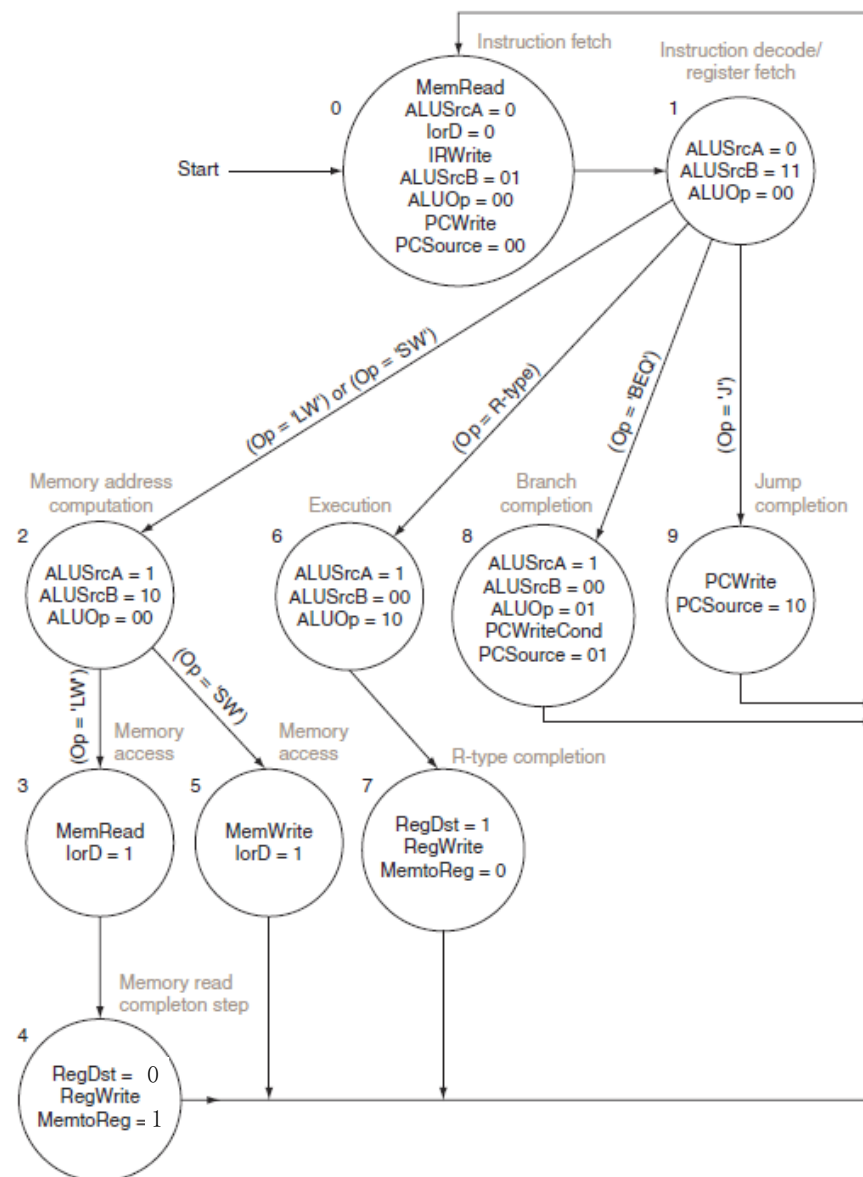

Implementing Finite-State Machine Control

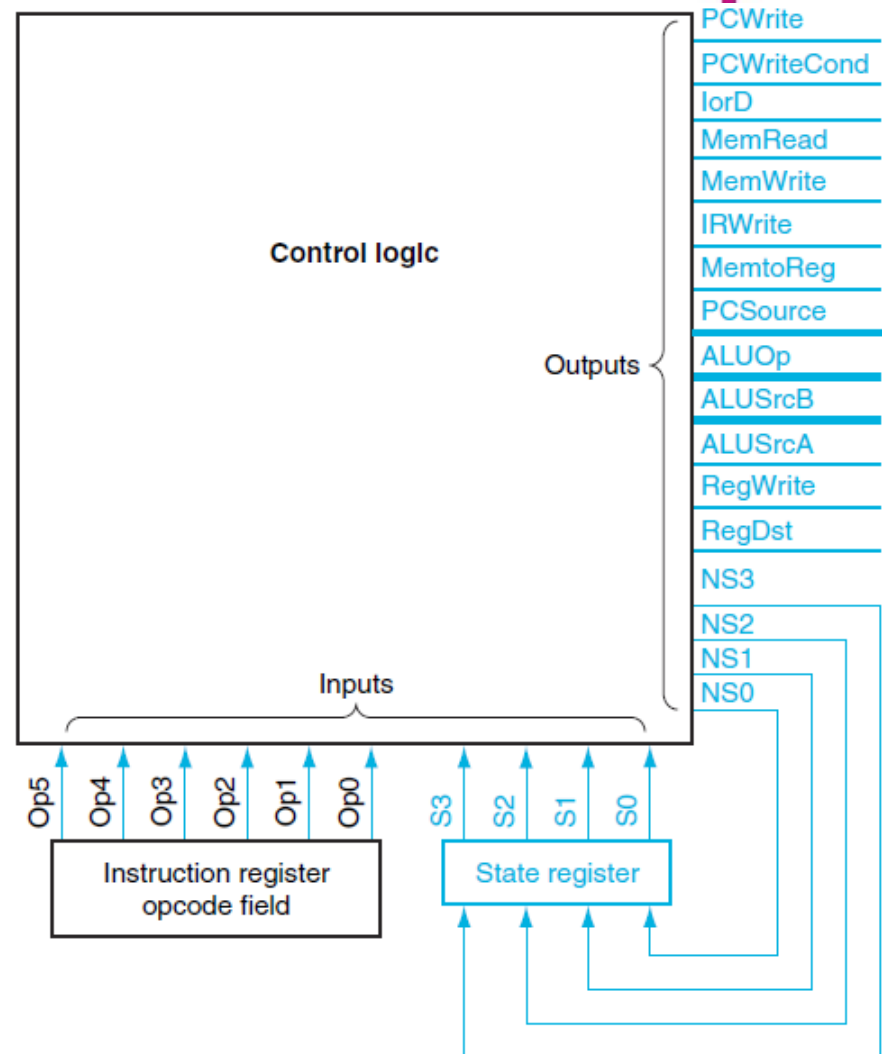- **State register** that holds the current state
 - S3, S2, S1, and S0
- **Combinational logic** block to compute the next state and output functions.



Control Truth Table

| Output | Current states | Op |
|-------------|--|---------------------------|
| PCWrite | state0 + state9 | |
| PCWriteCond | state8 | |
| lorD | state3 + state5 | |
| MemRead | state0 + state3 | |
| MemWrite | state5 | |
| IRWrite | state0 | |
| MemtoReg | state4 | |
| PCSource1 | state9 | |
| PCSource0 | state8 | |
| ALUOp1 | state6 | |
| ALUOp0 | state8 | |
| ALUSrcB1 | state1 + state2 | |
| ALUSrcB0 | state0 + state1 | |
| ALUSrcA | state2 + state6 + state8 | |
| RegWrite | state4 + state7 | |
| RegDst | state7 | |
| NextState0 | state4 + state5 + state7 + state8 + state9 | |
| NextState1 | state0 | |
| NextState2 | state1 | (Op = 'lw') + (Op = 'sw') |
| NextState3 | state2 | (Op = 'lw') |
| NextState4 | state3 | |
| NextState5 | state2 | (Op = 'sw') |
| NextState6 | state1 | (Op = 'R-type') |
| NextState7 | state6 | |
| NextState8 | state1 | (Op = 'beq') |
| NextState9 | state1 | (Op = 'jmp') |

Multi-Cycle Key Points

- Performance gain achieved from **variable-length** instructions
- $ET = IC * CPI * \text{cycle time}$
- Required very few new state elements
- More, and **more complex**, control signals
- Control requires **FSM**